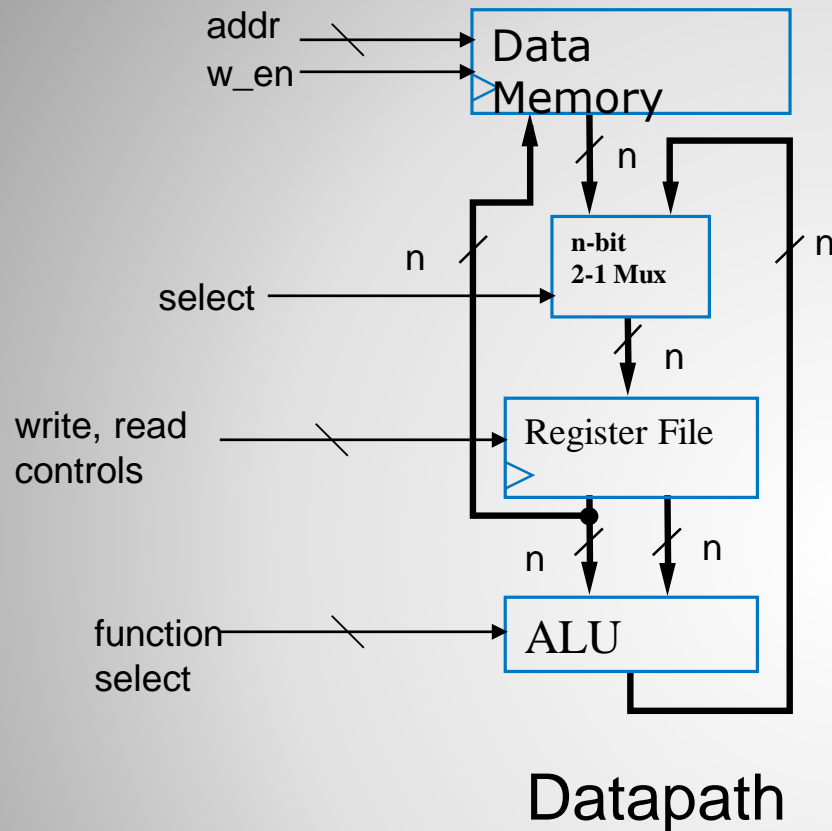


# **Programmable Processors**


- So far we've looked at 'hard-wired' or special purpose processors (like the SAD processor).
- We'll now look at programmable processors or 'stored program' processors.
- Different tasks can be performed by changing the program.
- Well-known examples: Pentium, PIC, ARM, Atmel AtMega, MIPS

## Programmable Processors




- Takes data from Data Memory
- Stores it in Register File
- Operates on it in ALU (puts it back into the Register File)
- Can store Register File data back into Data Memory
- Note the dual output Register File
- We've built every piece of this already


# Datapath Side

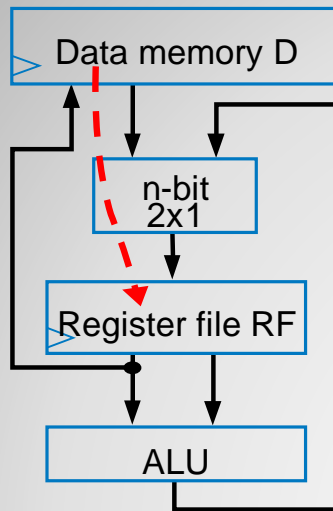

LOAD operation

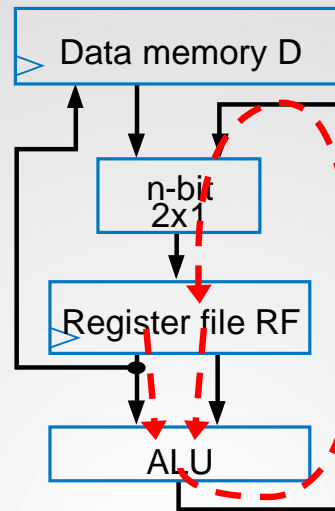

ALU operation  
(like an ADD)

 

STORE operation

$D[9] = D[0] + D[1]$  – requires a sequence of four datapath operations:

LOAD 0:  $RF[0] = D[0]$   
 LOAD 1:  $RF[1] = D[1]$   
 ADD 2:  $RF[2] = RF[0] + RF[1]$   
 STORE3:  $D[9] = RF[2]$


Each line here represents one instruction; so it takes four instructions to do this add

From F. Vahid's *Digital Design*

# Basic Datapath Operations

- $D[9] = D[0] + D[1]$  – requires a sequence of four datapath operations:
  - 0:  $RF[0] = D[0]$
  - 1:  $RF[1] = D[1]$
  - 2:  $RF[2] = RF[0] + RF[1]$
  - 3:  $D[9] = RF[2]$
- Each operation is an *instruction*
  - Sequence of instructions = *program*
  - Looks cumbersome, but that's the world of programmable processors – Decomposing desired computations into processor-supported operations
  - Store program in *Instruction memory*
  - *Control unit* reads each instruction and executes it on the datapath
    - PC: Program counter – address of current instruction
    - IR: Instruction register – current instruction

RF = Register File  
D = Data Memory

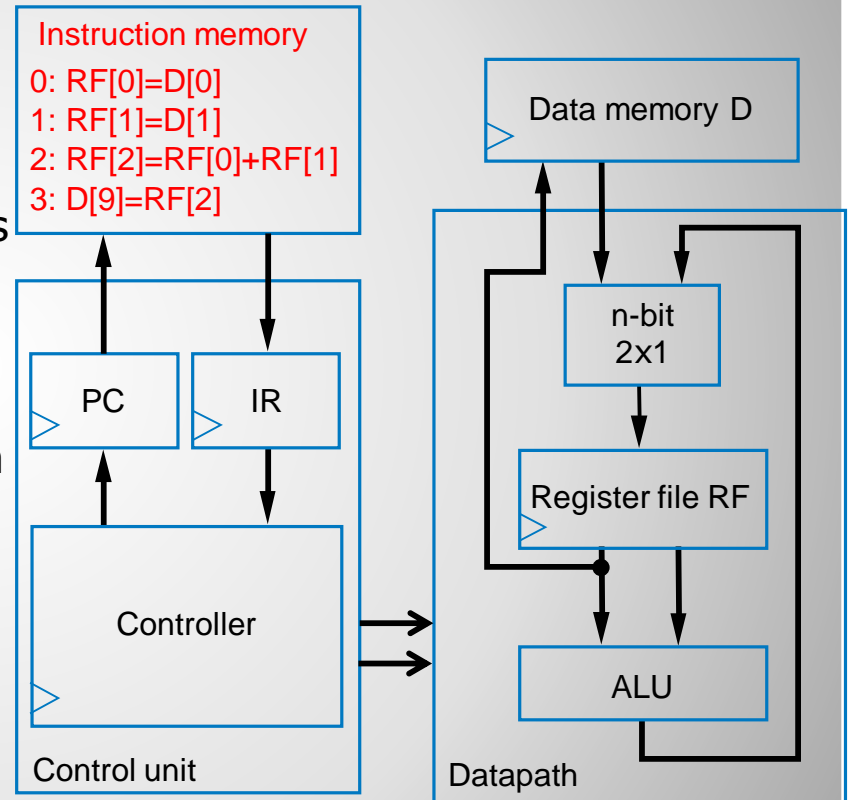


# Basic Architecture – Control Unit

From F. Vahid's *Digital Design*

- Data memory (RAM): 256 X 16
- Register file: 16 X 16 (dual output)
- ALU: Two 16-bit inputs, 16-bit output
- Instruction memory (ROM): 32 X 16


**The Size of Things**

## State Machine

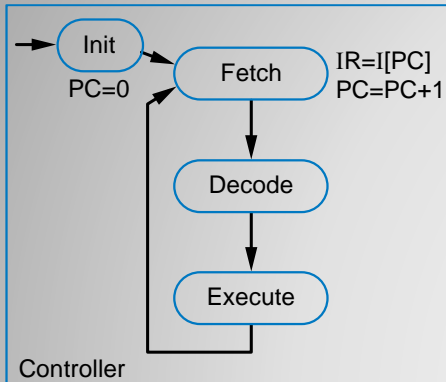

To summarize, the control unit processes each instruction in three stages:

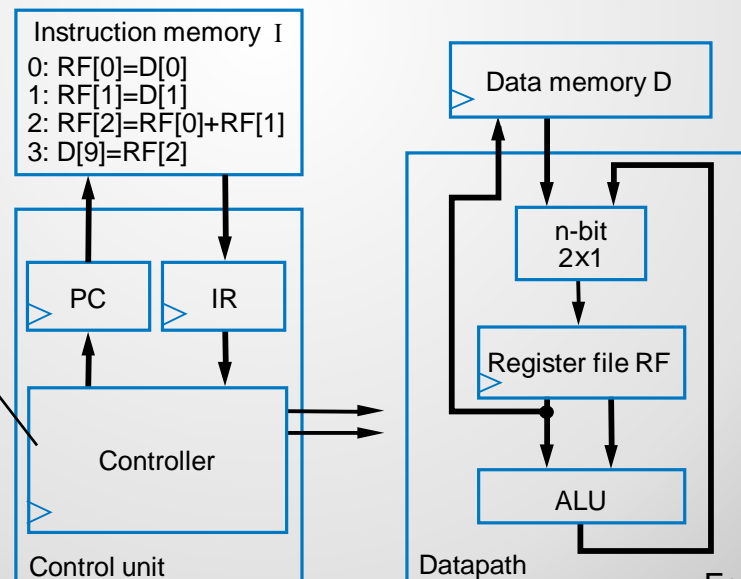1. first *fetching* the instruction by loading the current instruction into *IR* and incrementing the *PC* for the next fetch,
2. next *decoding* the instruction to determine its operation, and
3. finally *executing* the operation by setting the appropriate control lines for the datapath, if applicable. If the operation is a datapath operation, the operation may be one of three possible types:
  - (a) *loading* a data memory location into a register file location,
  - (b) transforming data using an *ALU* operation on register file locations and writing results back to a register file location, or
  - (c) *storing* a register file location into a data memory location.



From F. Vahid's *Digital Design*

# Basic Architecture – Control

- Instruction Set – List of allowable instructions and their representation in memory
- Each of our instructions is 16 bits long
- Most of them contain some address information
- General form : **operation source destination**

**NOOP** instruction – **0000 0000 0000 0000**

**STORE** instruction – **0001**  $r_3r_2r_1r_0$   $d_7d_6d_5d_4d_3d_2d_1d_0$

**LOAD** instruction – **0010**  $d_7d_6d_5d_4d_3d_2d_1d_0$   $r_3r_2r_1r_0$

**ADD** instruction – **0011**  $ra_3ra_2ra_1ra_0$   $rb_3rb_2rb_1rb_0$   $rc_3rc_2rc_1rc_0$

**SUBTRACT** instruction – **0100**  $ra_3ra_2ra_1ra_0$   $rb_3rb_2rb_1rb_0$   $rc_3rc_2rc_1rc_0$

**HALT** instruction – **0101 0000 0000 0000**

`r's are Register File locations (4 bits each)

`d's are Data Memory locations (8 bits each)

## Six-Instruction Processor



- **0000 0000 00000000**
- Always starts with **0000** (and contains nothing but zeros)
- Actually is just 0000 xxxx xxxxxxxx, since the 12 bits following 0000 are ignored.
- NoOp = No Operation
- Just takes up space (or time)
- Does not involve the Datapath
- If your program starts executing a string of 0s, nothing (too) bad will happen.

## NOOP Instruction

- **0001**  $r_3r_2r_1r_0$   $d_7d_6d_5d_4d_3d_2d_1d_0$
- Always starts with **0001**
- $r_3r_2r_1r_0$  is a 4-bit Register File address (source)
- $d_7d_6d_5d_4d_3d_2d_1d_0$  is a Data Memory address (destination)
- Moves 16 bits of data from the Register File to Data Memory
- Example: 0001 1111 0010 1001b (or 0x1F29) means "move the data at Register File 0xF (15d) to Data Memory location 0x29 (41d)"

## STORE Instruction

- **0010 d<sub>7</sub>d<sub>6</sub>d<sub>5</sub>d<sub>4</sub>d<sub>3</sub>d<sub>2</sub>d<sub>1</sub>d<sub>0</sub> r<sub>3</sub>r<sub>2</sub>r<sub>1</sub>r<sub>0</sub>**
- Always starts **0010**
- **d<sub>7</sub>d<sub>6</sub>d<sub>5</sub>d<sub>4</sub>d<sub>3</sub>d<sub>2</sub>d<sub>1</sub>d<sub>0</sub>** is a Data Memory address (source)
- **r<sub>3</sub>r<sub>2</sub>r<sub>1</sub>r<sub>0</sub>** is a 4-bit Register File address (destination)
- Moves 16 bits of data from Data Memory to the Register File
- Example : 0010 00001010 0111b (or 0x20A7) means "move the data at Data Memory location 0x0A (10d) to Register File 7."

## LOAD Instruction

- **0011 ra<sub>3</sub>ra<sub>2</sub>ra<sub>1</sub>ra<sub>0</sub> rb<sub>3</sub>rb<sub>2</sub>rb<sub>1</sub>rb<sub>0</sub> rc<sub>3</sub>rc<sub>2</sub>rc<sub>1</sub>rc<sub>0</sub>**
- Always starts with **0011**
- **ra<sub>3</sub>ra<sub>2</sub>ra<sub>1</sub>ra<sub>0</sub>** is a 4-bit Register File address (source for A)
- **rb<sub>3</sub>rb<sub>2</sub>rb<sub>1</sub>rb<sub>0</sub>** is a 4-bit Register File address (source for B)
- **rc<sub>3</sub>rc<sub>2</sub>rc<sub>1</sub>rc<sub>0</sub>** is a 4-bit Register File address (destination)
- Adds the 16 bits of A to 16 bits of B, stores the result in C (all these in the Register File)
- Example: 0011 0001 0010 0011b  
(or 0x3123) adds the data at Register File 1 to the data at Register File 2 and stores the result in Register File 3.

## ADD Instruction

- **0100** **ra<sub>3</sub>ra<sub>2</sub>ra<sub>1</sub>ra<sub>0</sub>** **rb<sub>3</sub>rb<sub>2</sub>rb<sub>1</sub>rb<sub>0</sub>** **rc<sub>3</sub>rc<sub>2</sub>rc<sub>1</sub>rc<sub>0</sub>**
- Always starts with **0100**
- **ra<sub>3</sub>ra<sub>2</sub>ra<sub>1</sub>ra<sub>0</sub>** is a 4-bit Register File address (source for A)
- **rb<sub>3</sub>rb<sub>2</sub>rb<sub>1</sub>rb<sub>0</sub>** is a 4-bit Register File address (source for B)
- **rc<sub>3</sub>rc<sub>2</sub>rc<sub>1</sub>rc<sub>0</sub>** is a 4-bit Register File address (destination)
- Subtracts the 16 bits of B from the 16 bits of A, stores the result in C (all these in the Register File)
- Example: 0100 0001 0010 0011b (or 0x4123) subtracts the data at Register File 2 from the data at Register File 1 and stores the result in Register File 3.

## SUBTRACT Instruction

- 0101 0000 00000000
- Always starts 0101 and remainder is all 0s
- Actually is 0100 xxxx xxxxxxxx, since all the bits following 0101 are ignored
- Causes the processor to just stop (**hard stop**)
- You need to reload it or reset it to get it going again.
- Does not involve the Datapath

## HALT Instruction

- Our program:

0: RF[0] = D[0]

1: RF[1] = D[1]

2: RF[2] = RF[0] + RF[1]

3: D[9] = RF[2]

4: HALT

- Becomes:

LOAD 0 0

LOAD 1 1

ADD 0 1 2

STORE 2 9

HALT


This is what gets  
stored in Instruction  
Memory



0x2000  
0x2011  
0x3012  
0x1209  
0x5000

or 0010 00000000 0000b  
or 0010 00000001 0001b  
or 0011 0000 0001 0010b  
or 0001 0010 00001001b  
or 0101 0000 00000000b

# First Program

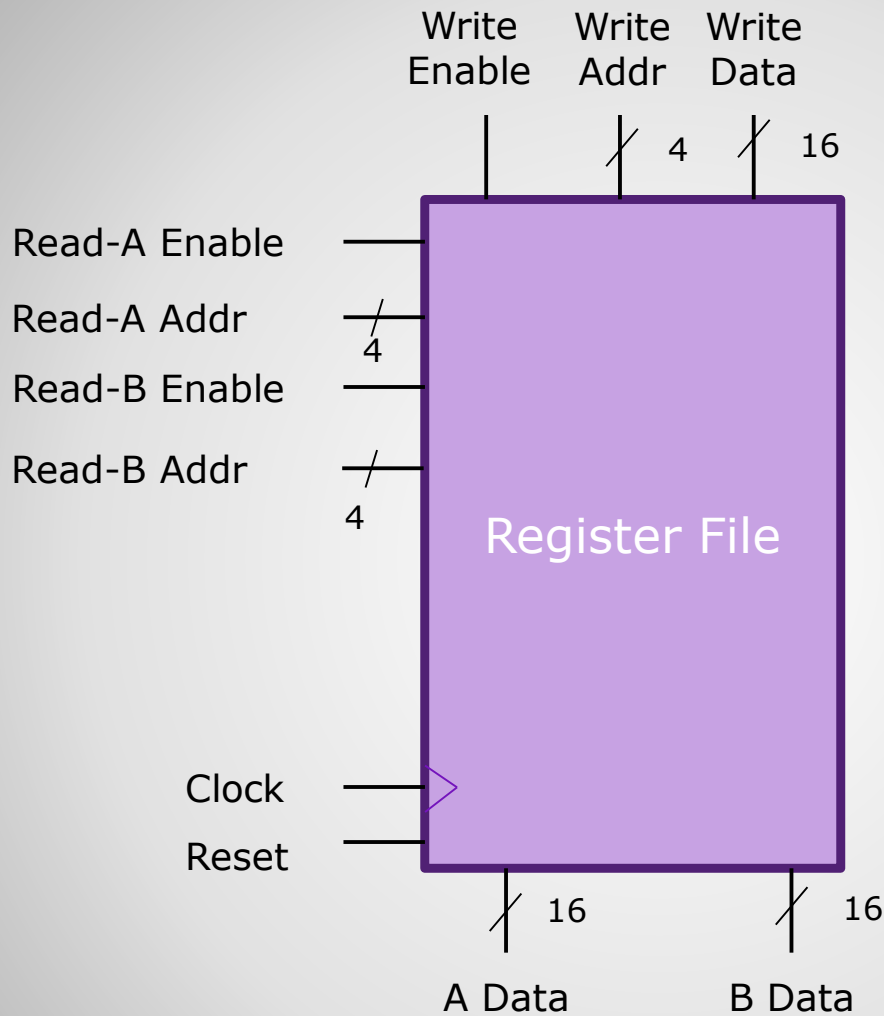

## The Register File (from HW6)



```
// This ALU has eight functions:
//   if s == 0 the output is 0
//   if s == 1 the output is A + B
//   if s == 2 the output is A - B
//   if s == 3 the output is A (pass-through)
//   if s == 4 the output is A ^ B
//   if s == 5 the output is A | B
//   if s == 6 the output is A & B
//   if s == 7 the output is A + 1;
// the additional functions are for future expansion
```


```
module ALU( A, B, Sel, Q );
  input [2:0] Sel;      // function select
  input [15:0] A, B;    // input data

  output [15:0] Q; // ALU output (result)
  ...
```

Alu\_s0 (function select)

3



Datapath

 

# The ALU (from HW6)



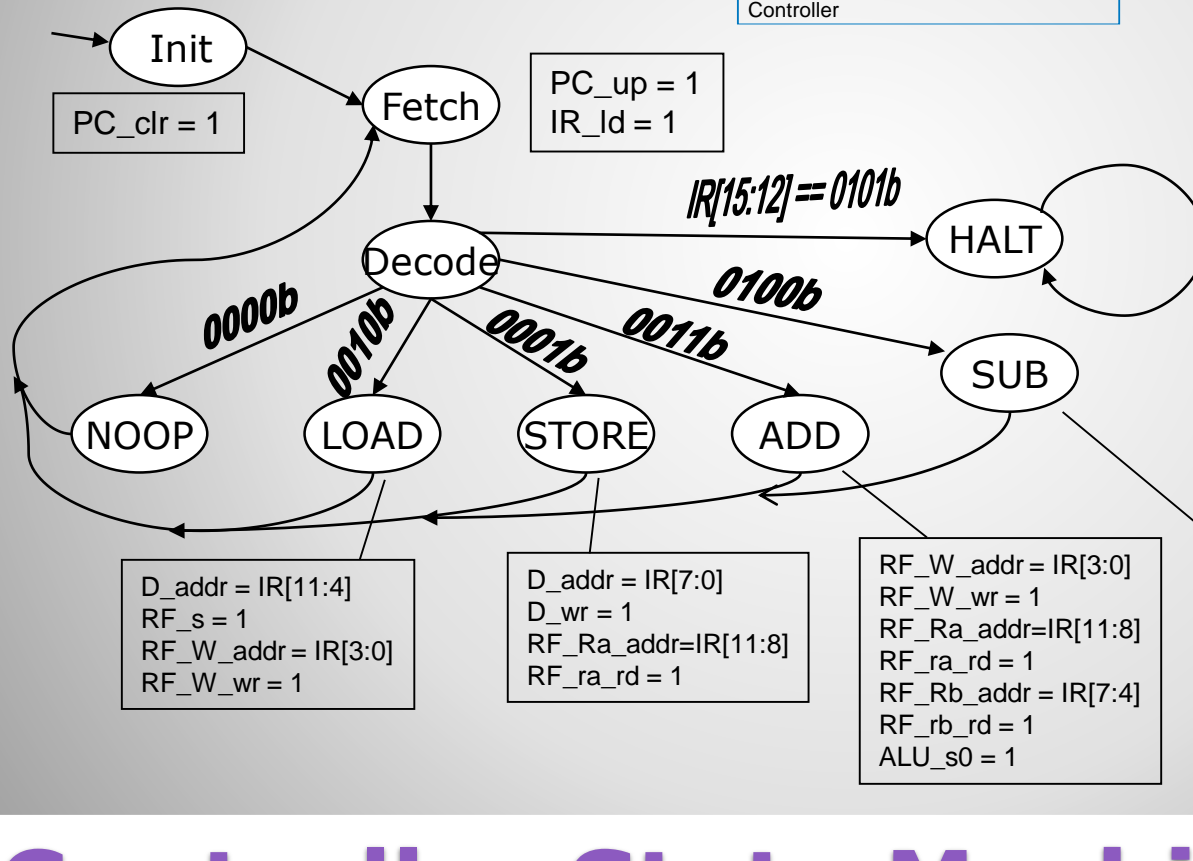 
# Control-Unit and Datapath for Our Programmable Processor



## Control Lines

Control	Size
PC_clr	1
PC_up	1
IR_Id	1
D_addr	8
D_wr	1
RF_s	1
RF_W_addr	4
RF_W_wr	1
RF_Ra_addr	4
RF_Ra_rd	1
RF_Rb_addr	4
RF_Rb_rd	1
Alu_s0	3

# Controller State Machine

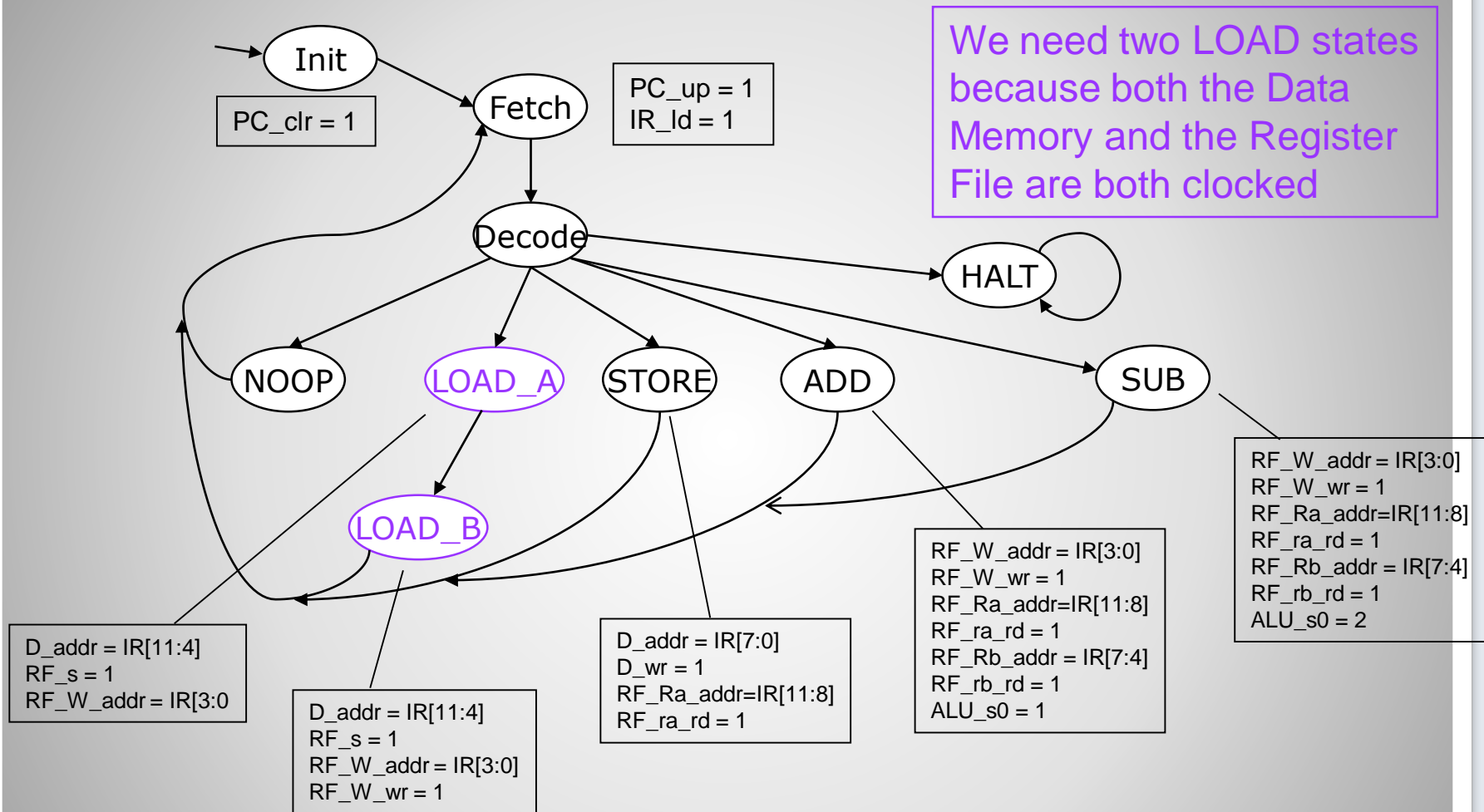


We need two LOAD states because both the Data Memory and the Register File are both clocked

# LOAD Anomaly

## 6.2 Architectural Overview


Figure 6-1. Block Diagram of the AVR Architecture

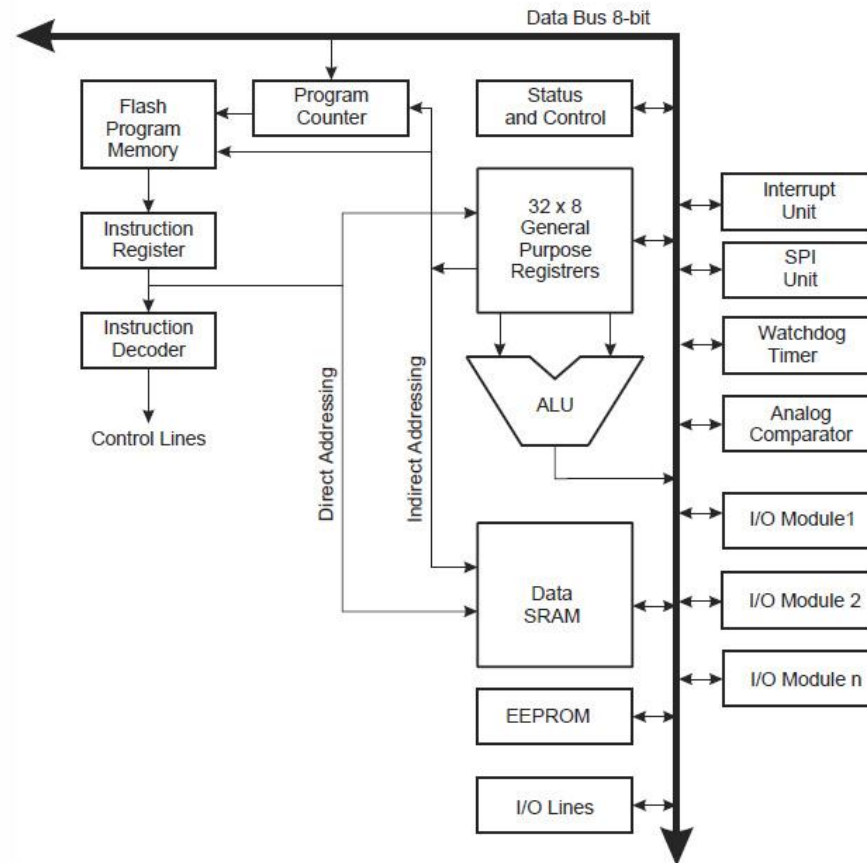

# ATMEL 168 Microprocessor
 
## Nios II Processor: The World's Most Versatile Embedded Processor


[Home](#) > [Devices](#) > [SoCs/Processors](#) > [Nios II](#)




### Related Links

- [What's New](#)
- [View Nios II Online Demos Now](#)
- [Buy a License](#)

# Altera's 'Soft' Processor

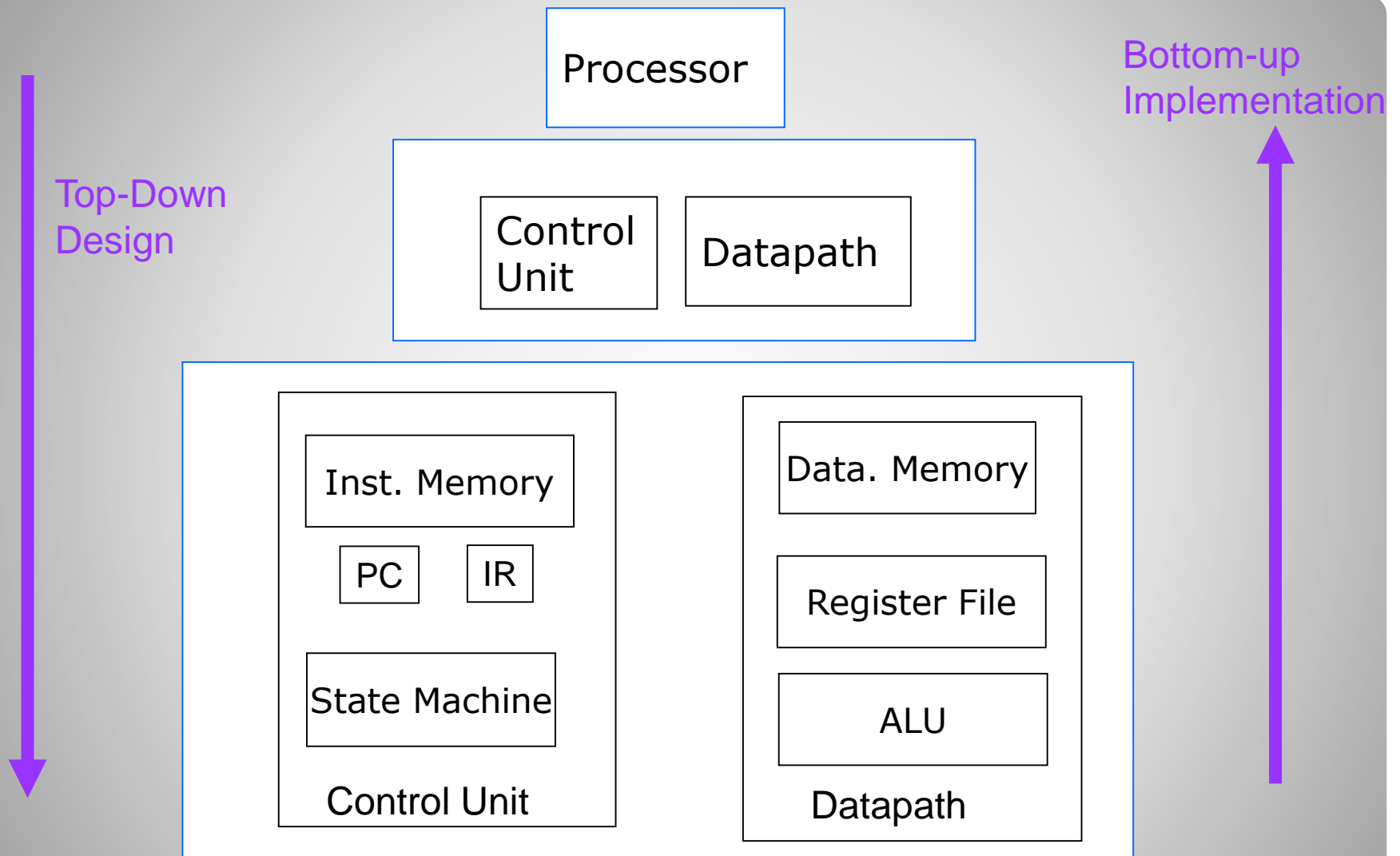


# Processor Module Layout

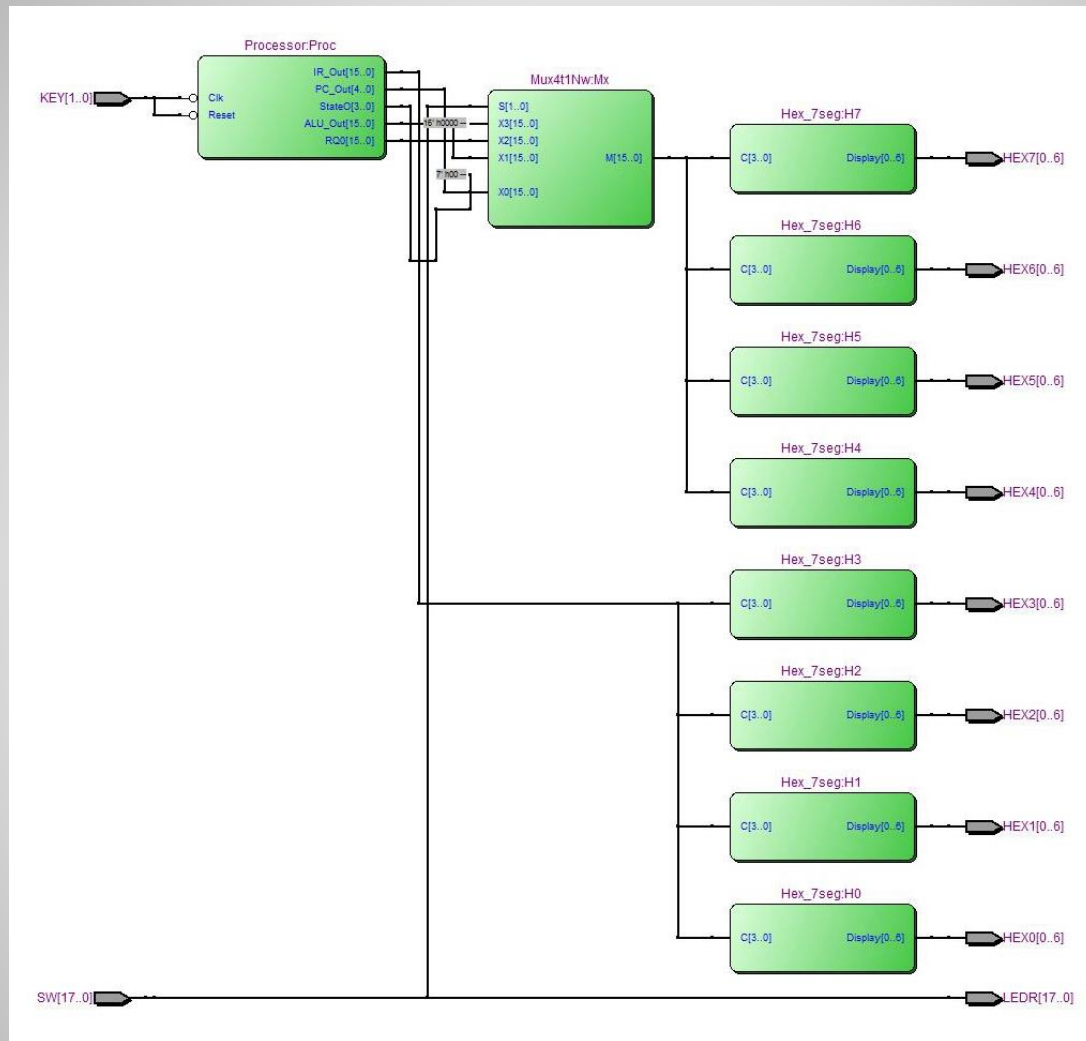

# Top Level


Note: Contains Extra Debug Information



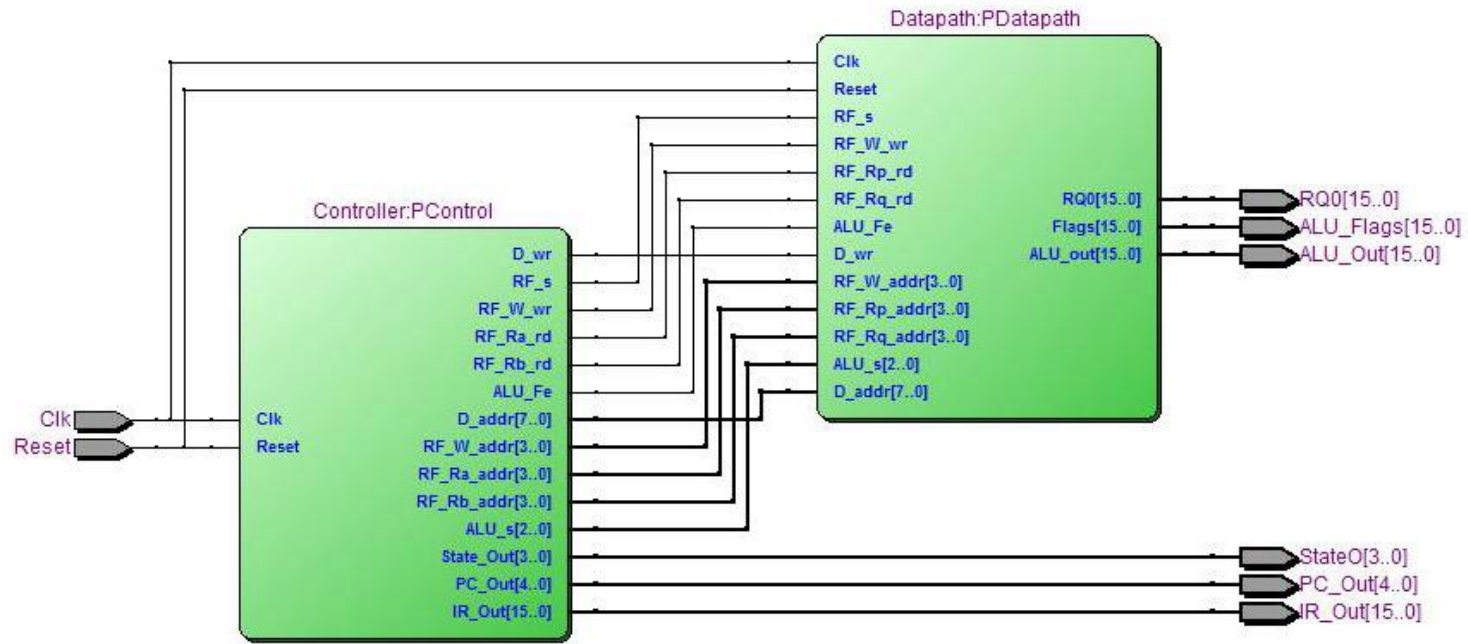


# Processor Level

Note: Contains Extra Debug Information

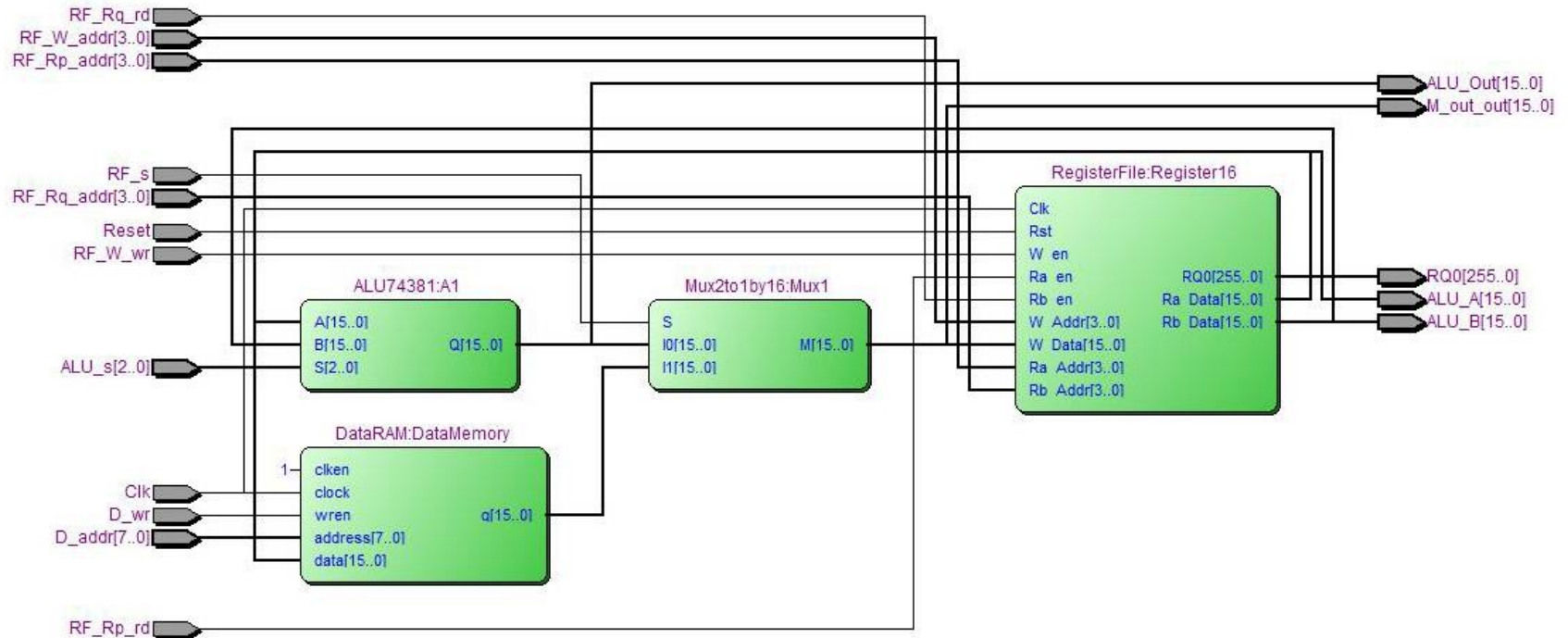

# Datapath Level

Note: Contains Extra Debug Information

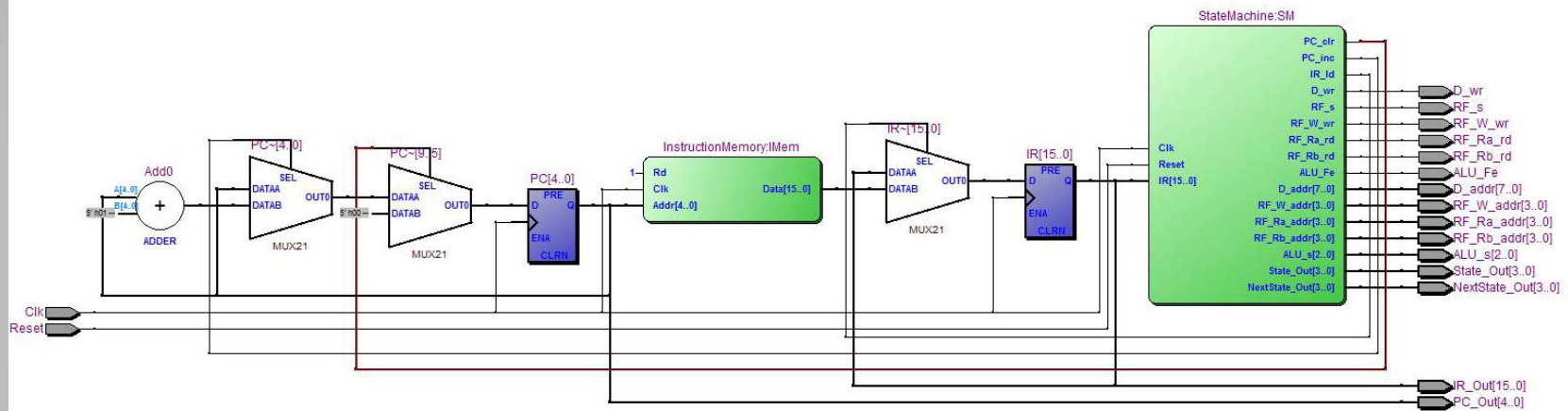

Note: Contains Extra Debug Information

# Controller Level

- Write a module (lowest level).
- TEST IT!
- Repeat until you have written all low-level modules.
- Make sure your state machine is recognized as such by Quartus
- Write the modules next level up (Control Unit, Datapath).
- TEST THESE!
- Write the Processor by instantiating Control Unit module and Datapath module and wiring them together.
- At this point you should be able to test your entire processor in ModelSim. Remember you will need to create a ModelSim project not just a work library since you are using LPMs.
- Final test for the Processor is running the program and inspecting Data Memory to make sure the correct value is stored in location 5.
- NOTE: You can do your unit testing on the DE2 or you can use ModelSim – It's probably better to test with ModelSim because you can more easily debug in this environment.

## Procedure